

11 detection:

Moore :

```
module lab4(clk,res,w,z,y,Y);
input clk,res, w;
output reg [1:0] y,Y;
output reg z;
parameter [1:0] A = 0, B = 1, C = 2;
always @(posedge clk, posedge res)
```

```
begin
  if (res == 1)
    begin
      y = 0;
      Y=0;
    end

  else
    begin
      y=Y;
      case(y)
        A:   if (w) Y= B;
        else Y= A;
        B:   if (w) Y = C;
        else Y = A;
        C:   if (w) Y = C;
        else Y = A;
      endcase
    end

  default: Y = 2'bxx;
endcase
end
end
```

```
always @(w, y)
begin
  case (y)
    A: z =0;
    B: z =0;
    C: z =1;
  endcase
end
endmodule
```

Mealy :

```
module lab4(clk,res, w, z,y,Y);
input clk, res, w;
output reg z;
output reg y,Y;
parameter A = 0, B = 1;
always @(posedge clk, posedge res)
begin
    if (res == 1)
        begin
            y = 0;
            Y=0;
            z=0;
        end

    else
        begin
            y=Y;
            case(y)

                A:    if (w)
                    begin
                        Y= B;
                        z=0;
                    end
                else
                    begin
                        Y= A;
                        z=0;
                    end

                B:    if (w)
                    begin
                        Y= B;
                        z=1;
                    end
                else
                    begin
                        Y= A;
                        z=0;
                    end

                default: Y = 1'bx;
            endcase
        end

    end
endmodule
```

2 states

```
module nowshin(clock, reset, cash_in, purchase, present_state, next_state, cash_return);
input clock, reset;
input [1:0] cash_in;
output reg purchase;
output reg [1:0] cash_return, present_state, next_state;
```

```
parameter      [1:0] state0= 2'b00, //0tk/final state
state1= 2'b01, //5tk state
state2= 2'b10, //10tk state
state3= 2'b11, //15tk state
n = 10, //price of my product
R0= 2'b00, //0tk return
R5= 2'b01, //5tk return
R10= 2'b10, //10tk return
R15= 2'b11; //15tk return
```

```
always@(posedge clock)
begin
```

```
if(reset==1)
begin
present_state = state0;
next_state = state0;
end
```

```
else
begin
present_state = next_state;
case(present_state)
```

```
state0: if(cash_in == 2'b00) // 0 tk
begin
next_state = state0;
purchase =0;
cash_return = R0;
end
```

```
else if(cash_in == 2'b01) // 5 tk
begin
next_state = state1;
purchase = 0;
cash_return = R0;
end
```

```

    else if(cash_in == 2'b10) // 10 tk
    begin
    next_state = state0;
    purchase = 1;
    cash_return = R0;
    end

    else if(cash_in == 2'b11) // 20 tk
    begin
    next_state = state0;
    purchase = 1;
    cash_return = R10;
    end


state1: if(cash_in == 2'b00) // 0 tk
    begin
    next_state = state0;
    purchase = 0;
    cash_return = R5;
    end

    else if(cash_in == 2'b01) // 5 tk
    begin
    next_state=state0;
    purchase = 1;
    cash_return = R0;
    end

    else if(cash_in == 2'b10) // 10 tk
    begin
    next_state=state0;
    purchase=1;
    cash_return = R5;
    end

    else if(cash_in == 2'b11) // 20 tk
    begin
    next_state = state0;
    purchase = 1;
    cash_return = R15;
    end


endcase
end
end
endmodule

```

3 states

```
module labb(clock, reset, cash_in, purchase, present_state, next_state, cash_return);
input clock, reset;
input [2:0] cash_in;
output reg purchase;
output reg [2:0] cash_return, present_state, next_state;

parameter      [1:0] state0= 2'b00, //0tk/final state
state1= 2'b01, //100tk state
state2= 2'b10, //200tk state

n = 300, //price of my product
R0= 3'b000, //0tk return
R100= 3'b001, //100tk return
R200= 3'b010, //200tk return
R300= 3'b011, //300tk return
R400= 3'b100; //400tk return

always@(posedge clock)
begin

if(reset==1)
begin
present_state = state0;
next_state = state0;
end

else
begin
present_state = next_state;
case(present_state)

state0: if(cash_in == 3'b000) // 0 tk
begin
next_state = state0;
purchase =0;
cash_return = R0;
end

else if(cash_in == 3'b001) // 100 tk
begin
next_state = state1;
purchase = 0;
cash_return = R0;
```

end

```
else if(cash_in == 3'b010) // 200 tk
begin
next_state = state2;
purchase = 0;
cash_return = R0;
end
```

```
else if(cash_in == 3'b011) // 300 tk
begin
next_state = state0;
purchase = 1;
cash_return = R0;
end
```

```
else if(cash_in == 3'b100) // 500 tk
begin
next_state = state0;
purchase = 1;
cash_return = R200;
end
```

```
state1: if(cash_in == 3'b000) // 0 tk
begin
next_state = state0;
purchase = 0;
cash_return = R100;
end
```

```
else if(cash_in == 3'b001) // 100 tk
begin
next_state = state2;
purchase = 0;
cash_return = R0;
end
```

```
else if(cash_in == 3'b010) // 200 tk
begin
next_state = state0;
purchase = 1;
cash_return = R0;
end
```

```
else if(cash_in == 3'b011) // 300 tk
begin
next_state = state0;
purchase = 1;
```

```
cash_return = R100;  
end
```

```
else if(cash_in == 3'b100) // 500 tk  
begin  
next_state = state0;  
purchase = 1;  
cash_return = R300;  
end
```

```
state2: if(cash_in == 3'b000) // 0 tk  
begin  
next_state = state0;  
purchase = 0;  
cash_return = R200;  
end
```

```
else if(cash_in == 3'b001) // 100 tk  
begin  
next_state = state0;  
purchase = 1;  
cash_return = R0;  
end
```

```
else if(cash_in == 3'b010) // 200 tk  
begin  
next_state = state0;  
purchase = 1;  
cash_return = R100;  
end
```

```
else if(cash_in == 3'b011) // 300 tk  
begin  
next_state = state0;  
purchase = 1;  
cash_return = R200;  
end
```

```
else if(cash_in == 3'b100) // 500 tk  
begin  
next_state = state0;  
purchase = 1;  
cash_return = R400;  
end
```

```
endcase  
end  
end  
endmodule
```