

Name: Nowshin Sumaiya
ID: 21301276
CSE460

Ans to the question no 1:

```
module number_two(clock, reset, cash_in, purchase, present_state, next_state, cash_return);  
input clock, reset;  
input [2:0] cash_in;  
output reg purchase;  
output reg [2:0] cash_return, present_state, next_state;  
parameter [1:0] state0= 2'b00, //0tk/final state  
state1= 2'b01, //100tk state  
state2= 2'b10, //200tk state
```

```
n = 120, //price product  
R0= 4'b0000,  
R20= 4'b0001,  
R40= 4'b0010,  
R80= 4'b0011,  
R100= 4'b0100,  
R120= 4'b0101,  
R180= 4'b0111,  
R380= 4'b1000,  
R420= 4'b1001,  
R480= 4'b1010;
```

```
always@(posedge clock)  
begin
```

```
if(reset==1)  
begin  
present_state = state0;  
next_state = state0;  
end
```

```
else  
begin
```

```
present_state = next_state;  
case(present_state)
```

```
state0: if(cash_in == 3'b000) // 0 tk  
begin  
next_state = state0;  
purchase = 0;  
cash_return = R0;  
end
```

```
else if(cash_in == 3'b001) // 40 tk  
begin  
next_state = state1;  
purchase = 0;  
cash_return = R0;  
end
```

```
else if(cash_in == 3'b010) // 100 tk  
begin  
next_state = state2;  
purchase = 0;  
cash_return = R0;  
end
```

```
else if(cash_in == 3'b011) // 200 tk  
begin  
next_state = state0;  
purchase = 1;  
cash_return = R80;  
end
```

```
else if(cash_in == 3'b100) // 500 tk  
begin  
next_state = state0;  
purchase = 1;  
cash_return = R380;  
end
```

```
state1: if(cash_in == 3'b000) // 0 tk
```

```
begin
next_state = state0;
purchase =0;
cash_return = R40;
end

else if(cash_in == 3'b001) // 40 tk
begin
next_state = state2;
purchase = 0;
cash_return = R0;
end

else if(cash_in == 3'b010) // 100 tk
begin
next_state = state0;
purchase = 1;
cash_return = R20;
end

else if(cash_in == 3'b011) // 200 tk
begin
next_state = state0;
purchase = 1;
cash_return = R120;
end

else if(cash_in == 3'b100) // 500 tk
begin
next_state = state0;
purchase = 1;
cash_return = R420;
end
```

```
state2: if(cash_in == 3'b000) // 0 tk
begin
next_state = state0;
purchase =0;
```

```
cash_return = R100;  
end
```

```
else if(cash_in == 3'b001) // 40 tk  
begin  
next_state = state0;  
purchase = 1;  
cash_return = R20;  
end
```

```
else if(cash_in == 3'b010) // 100 tk  
begin  
next_state = state0;  
purchase = 1;  
cash_return = R80;  
end
```

```
else if(cash_in == 3'b011) // 200 tk  
begin  
next_state = state0;  
purchase = 1;  
cash_return = R180;  
end
```

```
else if(cash_in == 3'b100) // 500 tk  
begin  
next_state = state0;  
purchase = 1;  
cash_return = R480;  
end
```

```
endcase  
end  
end  
endmodule
```

Ans to the question no 2:

```
module number_one(clk,res,w1,w2,w3,w4,z,y,Y); //moore
input clk,res, w1,w2,w3,w4;
output reg [2:0] y,Y;
output reg z;
parameter [2:0] A = 0, B = 1, C = 2, D=3, E=4;
always @(posedge clk, posedge res)

begin
    if (res == 1)
        begin
            y = 0;
            Y=0;
        end

    else
        begin
            y=Y;
            case(y)
                A:   if (w1) Y= B;

                else if (w2) Y= C;

                else if (w3) Y= B;

                else  if (w4) Y= C;

                B:   if (w1) Y= D;

                else  if (w2) Y= C;

                else  if (w3) Y= D;

                else  if (w4) Y= C;
```

C: if (w1) Y= B;

 else if (w2) Y= E;

 else if (w3) Y= B;

 else if (w4) Y= E;

D: if (w1) Y= D;

 else if (w2) Y= C;

 else if (w3) Y= D;

 else if (w4) Y= C;

E: if (w1) Y= B;

 else if (w2) Y= E;

 else if (w3) Y= B;

 else if (w4) Y= E;

default: Y = 3'bxx;

endcase

end

end

always @(w1,w2,w3,w4, y)

begin

 case (y)

 A: z =0;

 B: z =0;

 C: z =0;

 D: z =1;

 E: z =1;

```
    endcase  
end  
endmodule
```